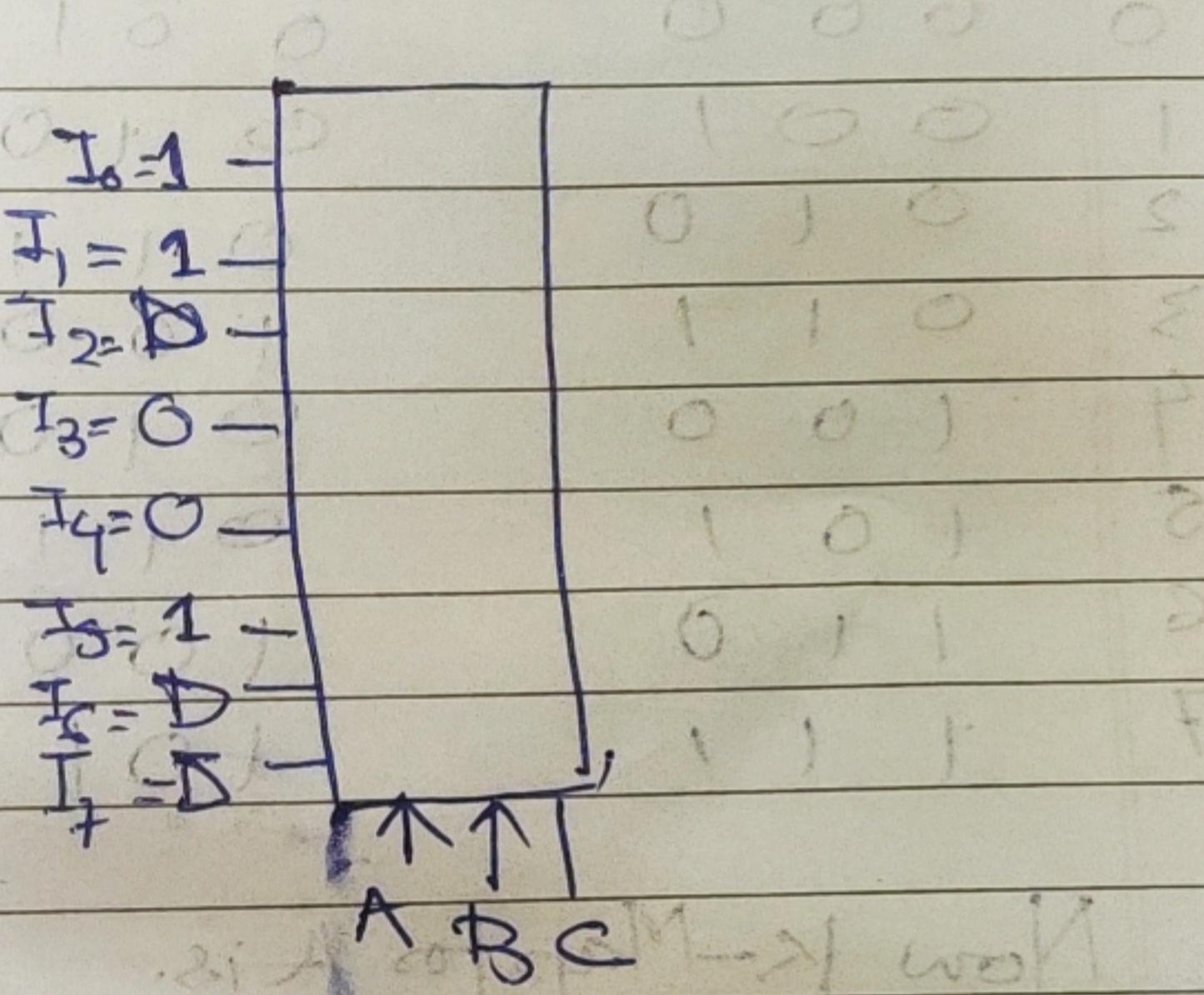


# COA Assignment

$$1. F = (A, B, C, D) = \Sigma m(1, 3, 5, 10, 11, 13, 14) + d(0, 2)$$

	A	B	C	D	F
0	0	0	0	0	X
1	0	0	0	1	1
2	0	0	1	0	X
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	1	0	0	0	0
8	0	1	1	1	0
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	0


Now the 8'MUX will be like



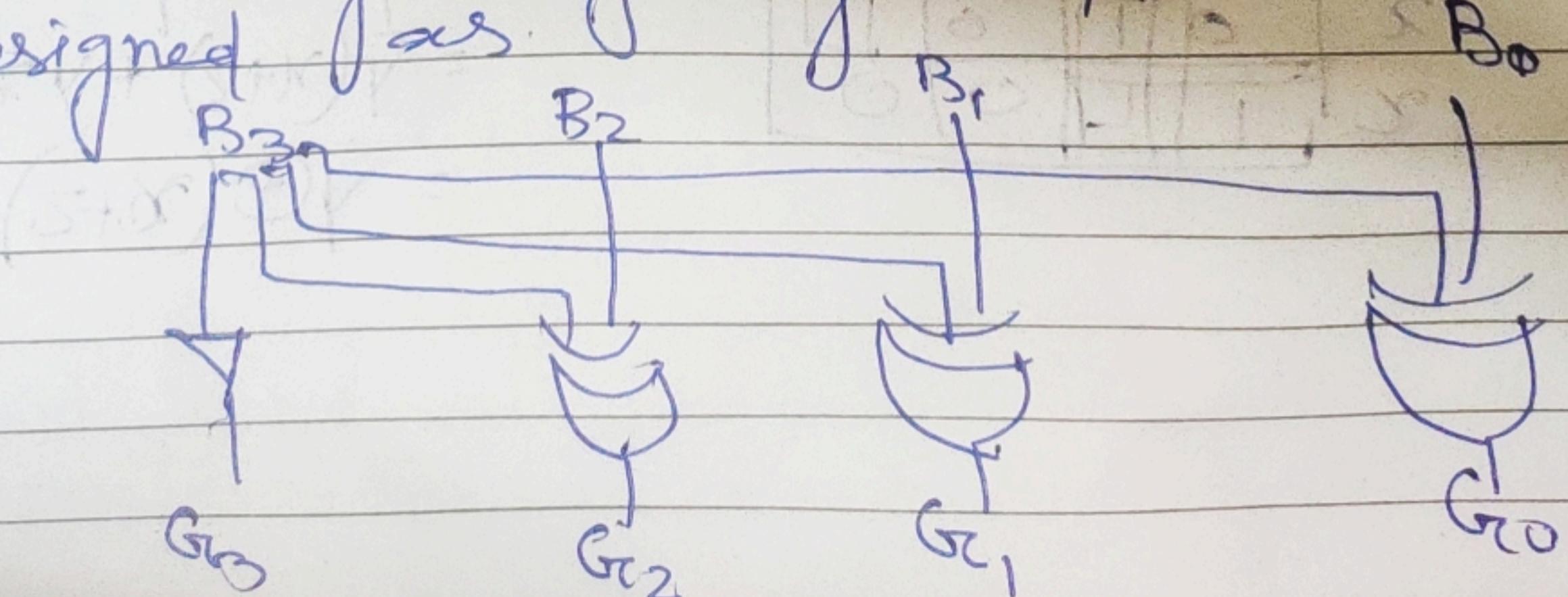2. Let the 4 bit binary no be denoted as  $B_3 B_2 B_1 B_0$

Where  $B_3$  is MSB

Where  $B_3$  is MSB  
As in Gray Code  $B_3$  is added to Rest  
of the digit neglecting carry, it can be  
designed as



Where the output  $G_3G_2G_1G_0$  is the Gray Code.

3. Given,

input  $x, y, z$  output - A, B, C

When binary input is 0, 1, 2, 3, the output is one greater when input is 4, 5, 6, 7 output is two less.

	$x$	$y$	$z$	$A$	$B$	$C$
0	0	0	0	0	0	1
1	0	0	1	0	1	0
2	0	1	0	1	1	1
3	0	1	1	0	0	0
4	1	0	0	0	1	0
5	1	0	1	1	1	1
6	1	1	0	1	0	1
7	1	1	1	0	1	1

Now K-Map for A is.

	$\bar{y}\bar{z}$	$\bar{y}z$	$yz$	$y\bar{z}$
$\bar{x}$	0	0	1	0
$x$	0	0	1	1

$$A = \bar{z}y + yz = y(\bar{z} + z) = y$$

Now K-Map for B is

	$\bar{y}\bar{z}$	$\bar{y}z$	$yz$	$y\bar{z}$
$\bar{x}$	0	1	0	1
$x$	1	1	0	0

$$\begin{aligned}
 B &= \bar{y}z + xy + \bar{x}y\bar{z} \\
 &= \bar{y}(x+z) + y\bar{x}\bar{z} \\
 &= y \oplus (x+z)
 \end{aligned}$$

Now K-Map for C is

classmate

Date \_\_\_\_\_

Page \_\_\_\_\_


	$\bar{y}\bar{z}$	$\bar{y}z$	$yz$	$y\bar{z}$
$\bar{x}$	1	1	0	1
$x$	0	1	1	0

$$C = \bar{x}\bar{z} + xz$$

$$= \bar{x}(x \oplus z)$$


$$= x \text{NOR } z$$

So the circuit will be like.

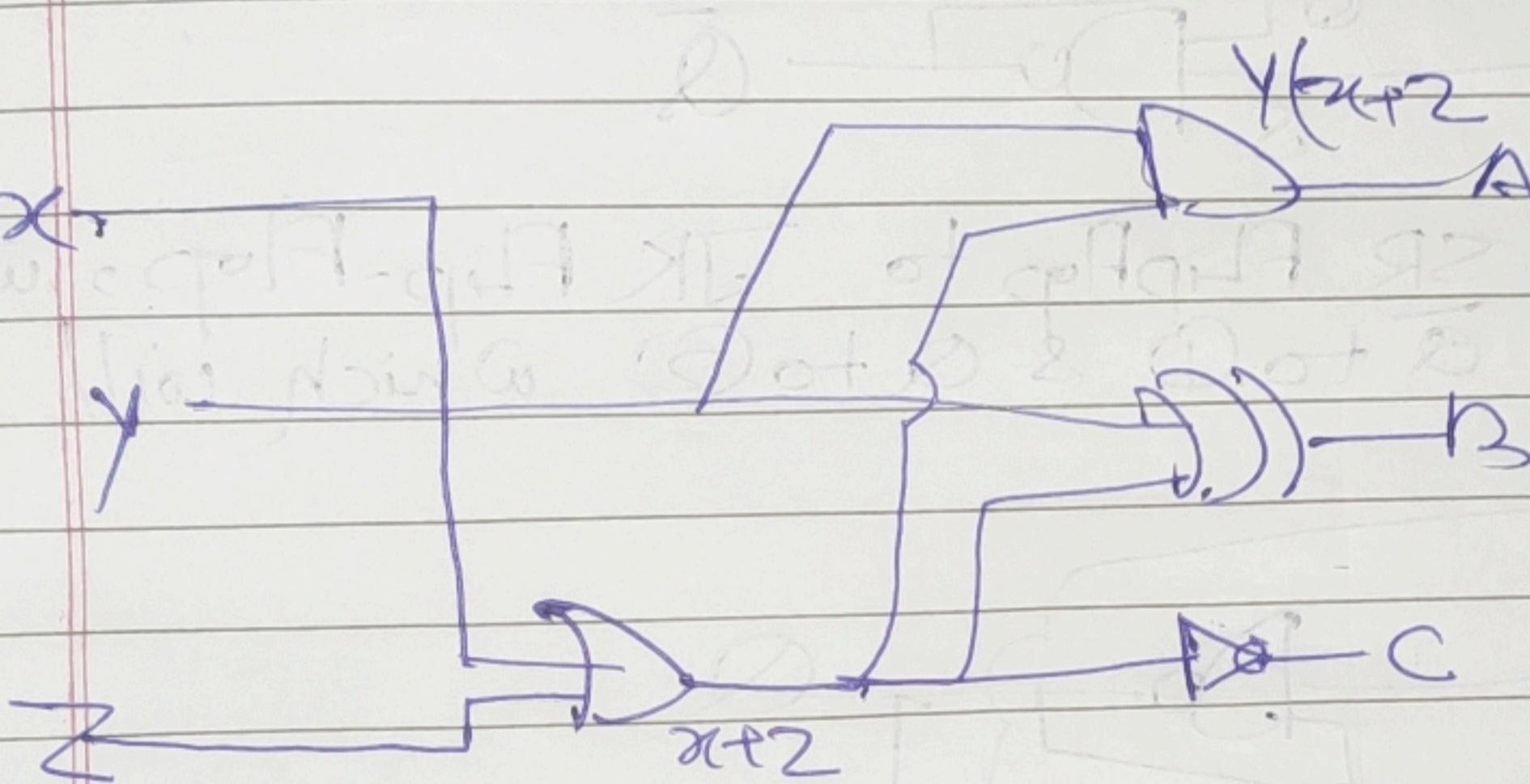


5) Connect SR FlipFlop to JK-FlipFlop.


SR FlipFlop is as follows

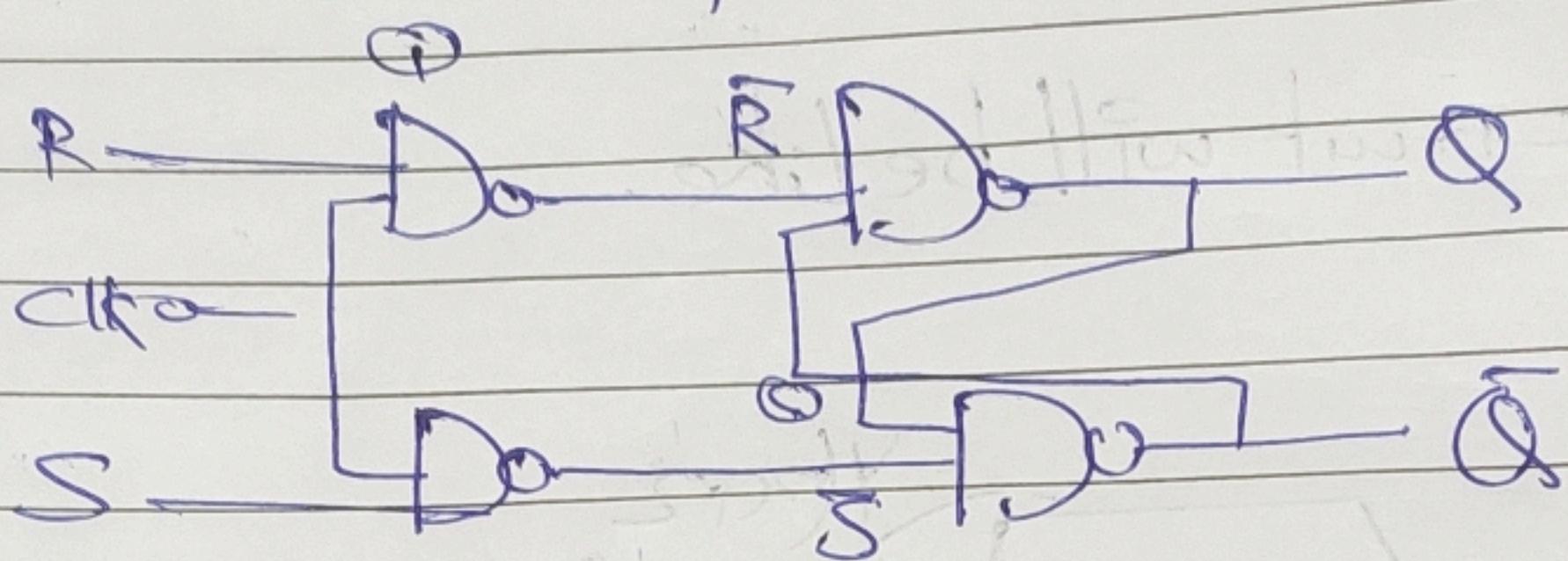

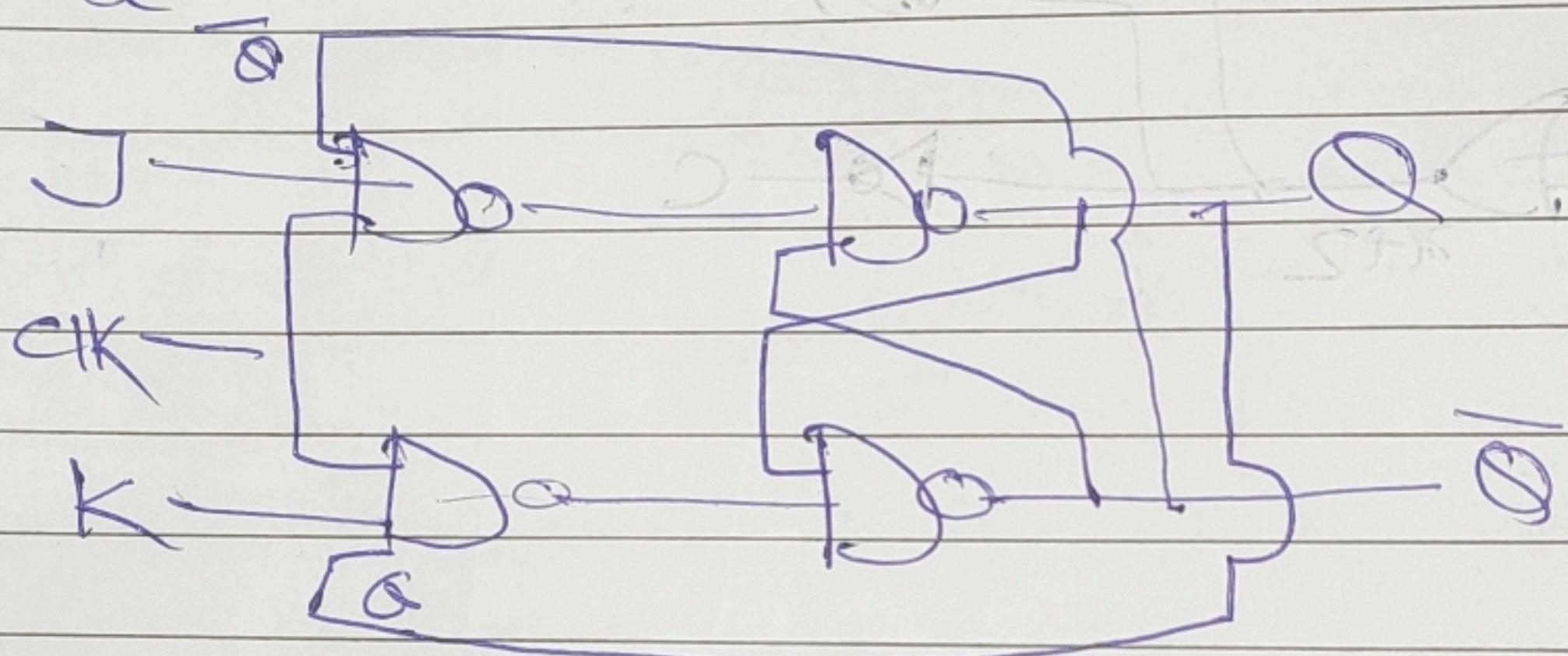To convert SR FlipFlop to JK Flip-Flop; we will connect  $\bar{Q}$  to  $J$  &  $Q$  to  $K$  which will be



⇒

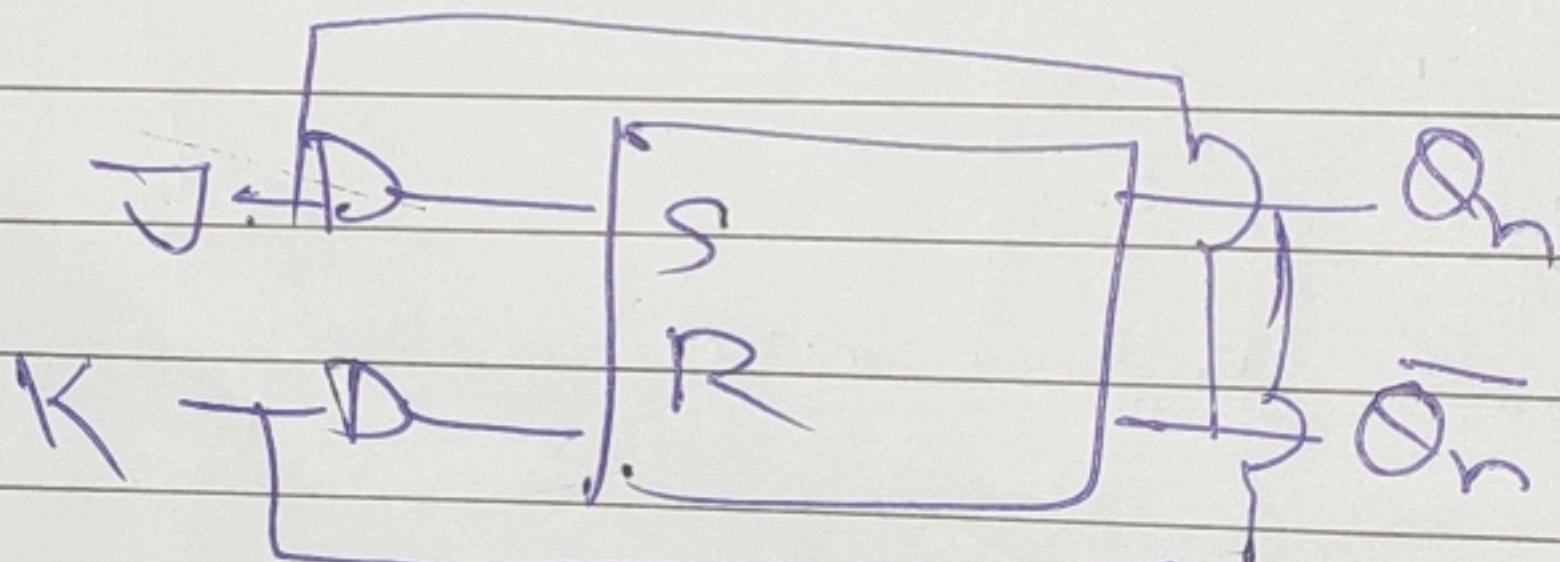

(6)  $5^*(-6)$  Using Booth's Algorithm

$$M = 0101$$

$$Q = 1010$$

count = 4

A

$Q_a$

$Q_b$

$Q_c$

0000

1010

0

0 Initial

0000

0101

0

1 ASR count = 3

1011

0101

0

A  $\leftarrow$  M

1101

1010

1

ASR count = 2

0010

1010

1

A  $\leftarrow$  M

0001

0101

0

ASR count = 1

1100

0101

0

A  $\leftarrow$  M

1110

0010

1

ASR out =

$$\therefore 5^*(-6) = 11100010$$

Q7  $R_1 \leftarrow \# 5$

Immedial Addressing

$R_1 \leftarrow M[500]$

Direct Addressing

$R_1 \leftarrow M[R_2]$

Indirect Addressing

Q.8 57 2 address instruction  $\Rightarrow 2^6 = 6$  bit

Max 1 address instruction  $= 2^6 - 1 = 3$

$= 2^3 - 1 = 7$  = one address

Q.8> Character equation of SR-Flip-Flop is as follows.

$Q_n$	SR	$Q_{n+1}$
0	0 0 0 0	0
1	0 1 0 1	0
2	0 1 0	1
3	0 1 1	not used
4	1 0 0 0	1
5	1 0 1	0
6	1 1 0	1
7	1 1 1	not used

Now K-maps for  $Q_{n+1}$

	SR	SR	SR	SR
$Q_n$	0 0 0 0	0 1 0 1	1 0 1 0	1 1 1 0
$Q_{n+1}$	0 0 0 1	0 1 1 1	1 0 1 1	1 1 1 1

$$Q_{n+1} = S + Q_n R$$

Characteristic equation of J-K flip-flop is as follows

$Q_n$	J	K	$Q_{n+1}$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Now K-map for  $Q_{n+1}$

	J	K	J	K	J	K		
$Q_n$	0 0 0 0	0 1 0 1	1 0 1 0	1 1 1 0	0 0 0 1	0 1 1 1	1 0 1 1	1 1 1 1
$Q_{n+1}$	0 0 0 1	0 1 1 1	1 0 1 1	1 1 1 1	0 0 1 0	0 1 0 1	1 0 1 0	1 1 1 0

$$Q_{n+1} = \overline{Q_n} J + Q_n K$$

The Drawback of SR flip-flop is that not all inputs are used in SR-Flip-Flop, when both S & R are 1, different output are obtained when we first take S then  $\bar{Q}$ , & when we first take  $\bar{Q}$  then Q. This Problem is fixed in JK flip-flop.

Q4. Characteristic equation of J-K Flipflop

$$Q_{n+1} = \bar{Q}_n J + Q_n K$$

$$J_A = x \quad K_A = B$$

$$J_B = \bar{x} \quad K_B = A$$

(a)  $Q_{n+1} = \bar{Q}_n J + Q_n K$

$$Q_{n+1} = \bar{A}_n x + A_n B$$

$$A(t+1) = \bar{A}(t)x + A(t)B$$

$$B(t+1) = \bar{B}(t)x + B(t)A$$

When  $x=0$  :  $A(t+1) = A_t B_t$

$$B(t+1) = \bar{A}_t B_t$$

When  $x=1$  :  $A(t+1) = \bar{A}_t + B_t A_t$

$$= \bar{A}_t + B_t$$


$$B_{t+1} = \bar{B}_t + B_t \bar{A}_t$$

$$= \bar{B}_t + \bar{A}_t = A_t B_t$$

State table

A	B	x	A(t+1)	B(t+1)
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	1	1
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	0

(b)

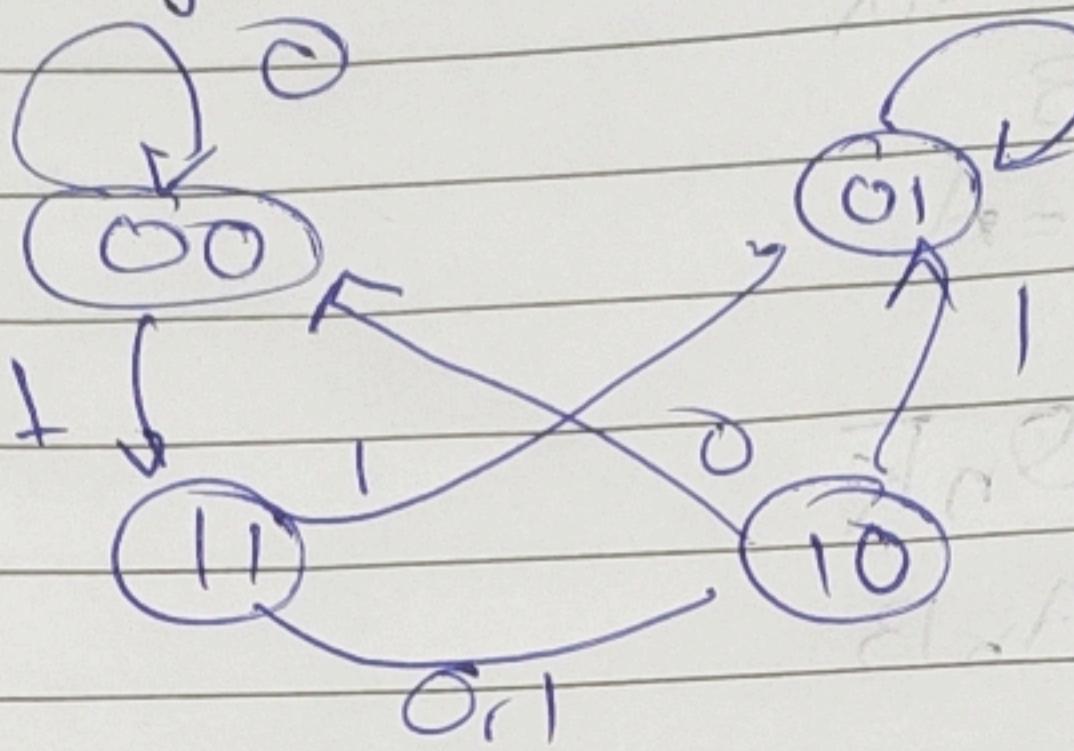State Diagram:

$$A(1)A + X(1)\bar{A} = (1+1)A$$

$$A(1)A =$$

$$\bar{A}A = 0$$

$$A(1)A + \bar{A}A = 1$$

Total stock

$$(1+1)A$$

0

1

1

0

1

0

$$(1+1)A \Rightarrow A$$

0

0

0

0

1

1

1

1

0

0

0

0

1

1

1

1

0

0

0

0

1

1

1

1